

CCM PFC demo board with 600 V CoolMOS™ S7 for active-line rectification and inrush current control

2400 W 65 kHz high-efficiency and high power density design

About this document

Authors

Matteo-Alessandro Kutschak

Alessandro Pevere

Franz Stueckler

Scope and purpose

This document is an application note describing the design and operation of a complete Infineon Technologies AG system solution for a 2400 W Continuous Conduction Mode (CCM) Power Factor Correction (PFC) converter with active-line rectification and solid-state relay solutions based on the 600 V CoolMOS™ S7.

The demo board presented in this document, later named as **EVAL_2K4W_ACT_BRD_S7** , has two additional features compared to a standard boost PFC:

- 1. Use of 600 V CoolMOS™ S7 for the active-bridge rectification to increase efficiency**
- 2. Replacement of inrush current relay with 600 V CoolMOS™ S7 to increase power density**

This document describes the converter hardware (shown in Figure 1) and the test results of the full Infineon solution, focusing on the main benefits of using the 600 V CoolMOS™ S7 for active-line rectification and relay replacement.

The main Infineon components used in the 2400 W active-bridge CCM PFC are described as follows:

Active bridge:

- 600 V CoolMOS™ S7 Superjunction (SJ) MOSFET
- IR11688S dual Synchronous Rectification (SR) control IC (Smartrectifier™)
- 2EDF7275F fast dual-channel functional isolated gate driver (EiceDRIVER™)

PFC:

- 600 V CoolMOS™ C7 SJ MOSFET
- 650 V CoolSiC™ Schottky diode
- Medium-power Schottky diode BAT165
- ICE3PCS01G standalone CCM PFC control IC
- 1EDN8550B single-channel with true differential inputs non-isolated gate driver (EiceDRIVER™)

Pre-charge:

- 600 V CoolMOS™ S7 SJ MOSFET

Bias supply:

- 950 V CoolMOS™ P7 SJ MOSFET
- ICE5QSAG CoolSET™ Quasi Resonant (QR) Flyback controller

Introduction

 


Figure 1 2400 W active-bridge CCM PFC based on 600 V CoolMOS™ S7

Intended audience

This document is intended for power supply designers, application engineers, students and anyone who wants to quickly improve the whole power range efficiency of a SMPS to achieve higher efficiency, such as that required by 80 PLUS Titanium, or to improve the thermal performance of power devices in high power density power supply units.

Table of contents

| | |
|--|-----------|
| 2400 W 65 kHz high-efficiency and high power density design | 1 |
| About this document..... | 1 |
| Table of contents..... | 3 |
| 1 Introduction | 4 |
| 1.1 Background and motivation | 4 |
| 1.2 System overview | 6 |
| 1.3 Main board description..... | 7 |
| 1.4 Daughter card description | 9 |
| 1.4.1 Active bridge..... | 9 |
| 1.4.1.1 Control method of the active-bridge line rectifier..... | 10 |
| 1.4.1.2 Active-bridge steady-state waveforms | 14 |
| 1.4.2 Bias power supply | 14 |
| 1.5 Board specification | 14 |
| 2 PFC efficiency increase with active bridge..... | 16 |
| 2.1 Theoretical efficiency improvement with active bridge | 16 |
| 2.1.1 Formula for calculating the conduction loss of bridge diodes and MOSFETs | 16 |
| 2.1.2 PFC efficiency estimation with active bridge | 17 |
| 2.2 PFC efficiency measurements with active bridge | 19 |
| 2.3 Relay MOSFET impact on PFC efficiency | 21 |
| 2.4 Temperature measurements | 21 |
| 3 DC-link pre-charge and PFC start-up..... | 25 |
| 3.1 Relay replacement introduction..... | 25 |
| 3.2 Pre-charge control strategy | 26 |
| 3.3 Pre-charge and start-up experimental results | 27 |
| 4 AC-Line Drop-Out (ACLDO)..... | 28 |
| 4.1 Test-bench..... | 28 |
| 4.2 Experimental results | 28 |
| 4.3 Simulation of body diode conduction during ACLDO..... | 30 |
| 5 Surge immunity test | 31 |
| 5.1 Surge specification from the standards | 31 |
| 5.2 Surge pulse test bench..... | 32 |
| 5.3 Surge pulse with AC-line | 33 |
| 5.3.1 Without active bridge..... | 33 |
| 5.3.2 With active bridge | 35 |
| 5.4 Influence of EMI filter on surge behavior..... | 36 |
| 6 Summary | 37 |
| 7 Schematics..... | 38 |
| 8 Bill of Materials (BOM) | 41 |
| 9 References | 46 |
| Revision history..... | 47 |

Introduction

1 Introduction

1.1 Background and motivation

Table 1 80 PLUS Titanium efficiency requirements classification

| 80 PLUS efficiency requirement | 115 V internal non-redundant (percent) | | | | 230 V internal non-redundant (percent) | | | |
|--------------------------------|--|----|----|-----|--|----|----|-----|
| | 10 | 20 | 50 | 100 | 10 | 20 | 50 | 100 |
| 80 PLUS Platinum | | 90 | 92 | 89 | | 90 | 94 | 91 |
| 80 PLUS Titanium | 90 | 92 | 94 | 90 | 90 | 94 | 96 | 91 |

In recent years, the trend for SMPS has been to increase both efficiency and power density at the same time with optimized cost.

A variety of efficiency requirements, such as 80 PLUS or EuP, are defined for various SMPS. Table 1 shows two examples of efficiency requirements for non-redundant internal power supplies, i.e. the 80 PLUS Platinum and the 80 PLUS Titanium PSU classes. In the Platinum class the PSU must have a peak efficiency above 94 percent at high-line and 92 percent at low-line, while for a Titanium design these values increase to 96 percent and 94 percent, respectively. In addition, some customers may define stricter efficiency requirements based on system operating conditions.

It is obvious that the overall efficiency of the PSU depends on both efficiency levels of the PFC and of DC-DC stages. For a fixed efficiency target of the PSU, if we are able to increase PFC performance than we can relax the requirements of the DC-DC converter and vice versa. Of course, this will impact the overall cost of the system. The question of every PSU manufacturer would be: what is the optimum balance between the two stages?

 


Figure 2 Reduction of DC-DC efficiency requirements for a PLUS Titanium design thanks to the active bridge (at 230 V_{Ac})

Introduction

 


Figure 3 Reduction of DC-DC efficiency requirements for an 80 PLUS Titanium design thanks to the active bridge (at 115 V_{Ac})

An easy and effective way of improving the PFC efficiency across the whole load and voltage range, without a big design impact, or increasing complexity and PFC cost, is to simply replace the classic diode bridge with an active bridge based on 600 V CoolMOS™ S7.

Figure 2 and Figure 3 clearly show the benefit of the active-bridge utilization in a standard CCM PFC. Targeting 80 PLUS Titanium efficiency, the simple replacement of the diode bridge with an active one, implemented with 22 mΩ 600 V CoolMOS™ S7, will reflect in a huge reduction of the peak efficiency that the DC-DC stage must guarantee in order to comply with Titanium class. A reduction of 0.6 percent can be seen at high-line and a reduction of 1 percent at low-line, meaning a potential increase of power density and reduction of the cost for the DC-DC stage.

The 800 W PFC developed by Infineon [1] is a good example of the achievable efficiency levels, for an 80 PLUS Platinum server design. However, if higher power is needed with the same form factor (thus increasing the power density) and even higher efficiency is required in order to achieve 80 PLUS Titanium level, the above mentioned design will no longer reach the targets.

This document introduces a 2400 W CCM PFC with active-bridge solution based on the new 600 V CoolMOS™ S7. The demo board has the same form factor as the one described in [1], meaning that the power density is three times higher. At the same time the efficiency is improved thanks to the replacement of the diode bridge with the active one. A full description of the prototype and experimental results will be presented in the following sections.

Introduction

1.2 System overview

 


Figure 4 2400 W active-bridge CCM PFC (EVAL_2K4W_ACT_BRD_S7) – simplified diagram showing the topology and the Infineon semiconductors used

Introduction

The simplified circuit diagram of the **EVAL_2K4W_ACT_BRD_S7** demo board is shown in Figure 4. The AC-DC converter is a 2400 W standard boost PFC working in CCM with two added features:

- Active-bridge line rectification for efficiency improvement
- Replacement of the Electro-Magnetic (EM) relay with a solid-state relay for power density increase

The active-line rectification is realized with a plug-in daughter card, named as **KIT_ACT_BRD_60R0xxS7** in Figure 4, based on the 600 V CoolMOS™ S7 in a TOLL package.

The classic bulky EM relay is replaced with a 600 V CoolMOS™ S7 (also in a TOLL package) in series with the bulk capacitor and parallelized with a NTC resistor for inrush current limitation.

The PFC stage is operated at both low-line (90 Vrms minimum, 120 Vrms nominal) and high-line (230 Vrms nominal, 265 Vrms maximum) in CCM with a 65 kHz fixed switching frequency. The bulk capacitance is designed to comply with typical hold-up time of 20 ms. The PFC controls the input AC current to a sinusoidal shape and the output DC voltage to a fixed DC value (around 390 V) by means of an easy-to-use analog controller.

The other daughter card, named as **KIT_6W_12V_P7_950V** , is employed to derive the 12 V power supply for the PFC controller, for the driving stage of the PFC switch and the solid-state relay. Finally, it is also used to supply the active-bridge daughter card.

The power supply has been designed to comply with the requirements of a data center server PFC stage targeting 80 PLUS Titanium efficiency and exceeding 80 W/in³ of power density.

1.3 Main board description

A 3D overview of **EVAL_2K4W_ACT_BRD_S7** , highlighting the main components, is reported in Figure 5. The board is 127 mm long, with a width of 85 mm and a height of 44 mm, thus complying with the target power density.

As shown by the demo board top view in Figure 5a, the design is highly compact as the placement of each component has been carefully optimized. All the Through-Hole Technology (THT) components are located on the top layer of the main PCB. The bias supply and active-bridge daughter cards can also be considered THT components.

Starting from the upper right side of Figure 5a, after the AC input connector (not visible in the 3D model), the fuse and the surge-protection Metal-Oxide Varistor (MOV) are placed together. They are followed by a two-stage EMI line filter. As already mentioned in the introduction, no input EM relay is employed for the inrush current limitation circuit, because in this demo board it is realized with a different concept. The removal of the bulky relay helps to increase the power density of the system. In the lower right side of the board, the active-bridge daughter card is soldered in parallel with the diode bridge. The latter is active only during high current transients, such as inrush current and surge conditions, while during normal PFC operation it is bypassed by the active bridge. The demo board is without heatsink on the diode bridge, as shown in Figure 1, as the diode bridge is not conducting continuous current. The user anyway has the possibility to mount the bridge heatsink in case the **EVAL_2K4W_ACT_BRD_S7** is tested with unplugged active bridge for efficiency comparison purposes. In the center part of the board we can find the PFC choke followed by the PFC diode (650 V CoolSiC™ Schottky G6) and PFC MOSFET (600 V CoolMOS™ C7). These two devices are instead cooled through a proper heatsink (removed for simplicity in Figure 5a but visible in Figure 1). Moving to the upper left side, the bulk capacitor is positioned horizontally in order to maximize component density. In series to it we find the NTC resistor, used for inrush current limitation. The bias supply daughter card is placed together with the output EMI filter and DC connector (element in green).

Active-bridge CCM PFC demo board based on 600 V CoolMOS™ S7

2400 W 65 kHz high-efficiency and high power density design



Introduction

The bias converter generates the required supplies for the driving and control circuitries. Furthermore, it offers the possibility of supplying the fan externally, not visible in Figure 5a. All the SMD components are located on the bottom layer, as shown in Figure 5b.

 


Figure 5 Placement of the different components in the 2400 W active-bridge CCM PFC with Infineon 600 V CoolMOS™ S7 MOSFET

Introduction

Starting from the upper right side of Figure 5b, the solid-state relay, implemented with a 600 V CoolMOS™ S7 in a TOLL package, is placed together with its driving circuitry. The latter will be discussed in detail in the surge pulse section, because it has been optimized for that condition. After the relay circuit, we can find the PFC analog controller (ICE3PCS01G) and the PFC MOSFET driver (1EDN8550B). On the bottom of Figure 4b, another two important elements are highlighted: the shunt resistor, used for PFC current control, and the bypass diode, active during surge transients.

1.4 Daughter card description

1.4.1 Active bridge

The active bridge daughter board is presented in Figure 6. The board is 35 mm long, with a width of 6 mm and a height of 30 mm, comparable to the size of a standard diode bridge rectifier (20 mm x 30 mm x 4.6 mm). This daughter board has five pins:

- Line (AC1) and neutral (AC2) alternate inputs
- Positive (V+) and negative (V-) rectified outputs
- Bias supply input (V_{CC})

The bias supply voltage of 12 V is provided by the PFC main board or by an external power supply, considering that the same V_{CC} is also used to supply PFC control and driving stages .

The daughter card integrates the power devices, the control and the driving components, thus enabling a high power density design. The power devices in a TOLL package are placed on the top side together with the gate resistors, as shown in Figure 6a. Further shrink of the board size is limited by safety distances among traces and components. On the bottom side, the controller (IR11688S) and the high-side MOSFETs driver (2EDF7275F) are placed as shown in Figure 6b. Additional components are: bootstrap R-C-D networks for high-side MOSFET driving and small-signal transistor in SOT-223 for extending the voltage capability of the controller. Without any additional transistor, the IR11688S drain voltage sense capability would be limited to 200 V. More details about the control of the active bridge will be discussed in the next subsection.

 


Figure 6 Placement of the different components in the active-bridge daughter card with Infineon 600 V CoolMOS™ S7 MOSFET: a) top view and b) bottom view

Introduction

1.4.1.1 Control method of the active-bridge line rectifier

 


Figure 7 Control concept of the active-bridge line rectification

Control of an active bridge for line rectification is intuitive. As shown in Figure 7, during the positive half-cycle of the mains, Q1 and Q4 are supposed to be switched on, while the others are kept off. Instead, during the negative half-cycle of the AC-grid, Q3 and Q2 are supposed to conduct, while the others are off.

It's important to highlight that all the MOSFETs are always conducting in the so-called "reverse mode" or "diode mode", with a positive current flowing from the source to the drain. In fact, the active bridge's purpose is to take over the conduction of the diode in order to achieve better efficiency, since MOSFET conduction losses are lower than those from diodes.

There are two possible ways of controlling the active-bridge switches:

1. By measuring the input voltage V_{AC}
2. By sensing the voltage drop across the MOSFET V_{DS}

In the *first method*, the control signal for each MOSFET of the active bridge is obtained by comparing the instantaneous input voltage (properly scaled down through a resistive divider) with a fixed reference voltage threshold (Figure 8). The voltage divider resistance should be high enough to minimize the quiescent loss, especially at high-line input. With this method, the on-time of the control signal at each cycle strongly depends on the input voltage level. This means that a shorter on-time is obtained at low-line input and vice versa.

 


Figure 8 First control method based on measuring the input voltage

Introduction

 


Figure 9 Second approach based on the SR controller

The *second approach* exploits the information of the current flowing through each low-side MOSFET by sensing the V_{DS} across the MOSFETs, as shown in Figure 9. This method is commonly used in the secondary-side SR controllers. Such a solution is already available in the market and is widely used in high-efficiency step-down DC-DC converters, for example for driving the SR of an LLC resonant converter.

This second method is the one employed in the proposed active-bridge daughter card by using Infineon controller IR11688S, as shown in Figure 10.

The IR11688S is a dual smart secondary-side controller IC optimized to drive two N-channel power MOSFETs configured for SR in resonant converter applications, with drain voltage sensing capability up to 200 V. Small-signal transistors T1 and T2 in Figure 10 are added to further extend the voltage capability of the controller, matching the high-line PFC application.

The drain-to-source voltage of the low-side MOSFET (Q3, Q4) of the active bridge is sensed through the VD1 and VD2 pins to determine the source-to-drain current and consequently turn on/off each gate rapidly at the start/end of each conduction cycle. The drain-to-source voltages are compared to different thresholds to precisely control the gates, as shown in Figure 11a.

Introduction

 


Figure 10 Adaptation of IR11688S for active-line rectification

Turn-on blanking time

When the conduction phase of each active full-bridge MOSFET begins, the active MOSFET is still off, therefore the current starts to flow through the body diode, producing a negative V_{DS} voltage across it, as shown by the blue line in Figure 11b. The body diode's voltage drop is sufficient to trigger the turn-on threshold V_{TH2} (≈ -230 mV). If V_{DS} remains below V_{TH2} for more than T_{Don} (≈ 150 ns), the gate of the corresponding active MOSFET is driven high, which causes V_{DS} to reduce rapidly to $I_D * R_{DS,ON}$. The internal delay timer will be reset if V_{DS} rises above V_{TH2} before T_{Don} times out. This turn-on blanking time represents the body diode conduction time and helps to avoid mis-firing that could be triggered by high-frequency ringing in Discontinuous Conduction Mode (DCM) operation. For fixed-frequency 50/60 Hz PFC applications this means very high duty cycle for the active bridge, regardless of working at low- or high-line.

Minimum on-time

The voltage drop at the gate turn-on is usually accompanied by some amount of ringing, which could potentially trigger the input comparator to turn off the gate drive very quickly. However, the Minimum On-Time (MOT) blanking period prevents this. For fixed-frequency 50/60 Hz PFC applications the MOT is rather to be set to the highest possible value, through the value of R15 of Figure 10. This results in $T_{MOT} = R_{MOT} * 2 * 10^{-11} + 20ns \approx 2us$.

Regulation phase

At the end of the MOT, the gate output is no longer driven high and reverts to a high impedance state. When V_{DS} is below the regulation threshold V_{THR} (≈ -40 mV), a weak pull-down gradually discharges the gate voltage held by the active-bridge MOSFET input capacitance. As the gate voltage drops, the MOSFET channel resistance increases as it enters the linear region. This causes V_{DS} to once again exceed V_{THR} so that weak pull-down will cease until the conduction current falls to the point where V_{DS} again drops below V_{THR} .

Introduction

 


Figure 11 Behavior of IR11688S: a) input comparator thresholds and b) example of waveforms

This regulating process continues so that the conduction period is extended until the current has fallen to a very low level. In this way premature turn-off, which can arise due to parasitic inductances in PCB traces and the MOSFET package, is prevented. This period of conduction through the SR MOSFET body diodes is thereby reduced to a minimum, improving overall system efficiency.

Turn-off and reset

At the end of the switching cycle the conduction rectifier current reduces to zero so the V_{DS} voltage will cross the turn-off threshold V_{TH1} (≈ -4 mV). When this happens the gate is driven low to switch off the SR MOSFET. Any residual current will again start flowing through the body diode, causing a negative step in V_{DS} . When this occurs V_{DS} could potentially trigger turn-on once again by crossing V_{TH2} . To prevent this possibility, turn-on is blanked for a time period t_{DBLANK} (≈ 15 μ s) after turn-off has occurred. The blanking time is internally set and can be reset only when V_{DS} crosses the positive threshold V_{TH3} (≈ 1.18 V). Reset occurs only when V_{DS} remains higher than V_{TH3} for more than the reset blanking time, t_{BRST} (≈ 400 ns). This protects against false triggering due to ringing after the turn-off phase. Once reset the IR11688S is re-armed so that turn-on may be triggered for the next conduction cycle.

Reset V_{TH3} and regulation V_{THR} thresholds are referenced to GND (see [3]), therefore they cannot be changed by any circuit modification. On the other hand, turn-on V_{TH2} and turn-off V_{TH1} thresholds are referenced to V_S , thus giving the designer freedom to change them by adapting the resistor-divider (named as “Source level shifter” in Figure 10). In our example we are shifting the V_S voltage of around 40 mV. This V_S offset has to be adapted depending on the MOSFET $R_{DS,ON}$ and the application.

The IR11688S has very low quiescent current when the gate drivers are not switching to offer minimal power consumption in standby mode (less than 500 μ A).

Introduction

1.4.1.2 Active-bridge steady-state waveforms

Figure 12 shows the steady-state waveforms of active-bridge low-side complementary driving signals during PFC operation at high-line.

 


Figure 12 Steady-state waveforms of active-bridge low-side complementary driving signals (magenta and light blue lines), input current and voltage (yellow and green lines) and PFC output voltage (light blue line) at 230 V_{AC}

1.4.2 Bias power supply

For details of the bias power supply daughter card please refer to [2].

1.5 Board specification

Table 2 presents the specification of the 2400 W active-bridge PFC developed using the 600 V CoolMOS™ S7 in a TOLL package.

Introduction

Table 2 Summary of specifications and test conditions for the 1600 W PSU

| Parameter | Condition | Specification |
|------------------------------------|--|-------------------------------|
| Input voltage range | | 90 to 265 Vrms |
| Nominal input voltage at low-line | | 115 Vrms |
| Nominal input voltage at high-line | | 230 Vrms |
| AC-line frequency range | | 45 to 65 Hz |
| Max. ambient temperature | | 40°C |
| Max. input current | 90 V _{AC} /1200 W | 14 Arms |
| Inrush current | 230 Vrms, 50 Hz/60 Hz, measured on the first AC cycle | i_{in_peak} less than 30 A |
| Power Factor (PF) | More than 20 percent of load | More than 0.95 |
| Hold-up time | $P_{out_max} = 1800\text{ W}/V_{out_min} = 311\text{ V}$ | 10 ms |
| Nominal output voltage | | 390 V |
| Max. output power | 230 V _{AC} | 2400 W |
| Peak efficiency at high-line | 230 V _{AC} | More than 98.6 percent |
| Peak efficiency at low-line | 115 V _{AC} | More than 97.6 percent |

2 PFC efficiency increase with active bridge

2.1 Theoretical efficiency improvement with active bridge

 


Figure 13 Power dissipation of power devices with a 1000 W PFC circuit at 85 V_{AC} and 230 V_{AC}

A SMPS, with traditional PFC and an efficient enough DC-DC converter, can quite easily meet the 80 PLUS Platinum efficiency requirements. In order to achieve greater efficiency, such as 80 PLUS Titanium, maintaining the same circuit structure with some efficiency improvements will not be sufficient. By only replacing the power components with better ones, for example using a MOSFET with lower $R_{DS,ON}$ or an inductor with less core material loss, it is almost impossible to achieve adequate efficiency improvements in the whole voltage and load range.

Figure 13 shows the power losses of main components in a 1000 W standard PFC circuit. The bridge rectifier’s power dissipation dominates among power losses, regardless of low-line or high-line input voltage.

Reducing the power dissipation of a bridge rectifier is the simplest and most effective way to improve efficiency. In the following section, a comparison between conduction losses of diodes and active bridges is described in detail.

2.1.1 Formula for calculating the conduction loss of bridge diodes and MOSFETs

The advantage of active-bridge line rectification for power supply is not only to improve the efficiency from light load to full load, but also to reduce the temperature of the power device. To estimate the efficiency improvement achieved by active-bridge line rectification, the power dissipation of a bridge rectifier and power MOSFET needs to be calculated first.

The equivalent diode circuit is derived as a DC potential, V_T , in series with an equivalent resistance, R_D , as shown in Figure 14. The formula for conduction loss of the diode is:

$$P_{con} = V_T \times I_{D,avg} + I_{D,rms}^2 \times R_D (@specified T_j)$$

Where $I_{D,avg}$ and $I_{D,rms}$ is the average current and effective current of the diode, respectively.

Moreover, the MOSFET can be modeled as a resistance, which is the $R_{DS,ON}$ at a specified junction temperature. The conduction loss of the MOSFET can be calculated by:

$$P_{con} = I_{D,rms}^2 \times R_{DS,ON} (@specified T_j)$$

PFC efficiency increase with active bridge

 


Figure 14 The equivalent circuit and the conduction loss of the diode

Theoretically, it is simple to calculate the power loss improvement by subtracting the power dissipation of the MOSFET from that of the bridge rectifier. The efficiency improvement can be obtained from the power loss reduction at different load conditions. However, it is not simple in real calculations for the following reasons:

- a. The equivalent circuit of diode power dissipation is considered as DC potential in series with an equivalent resistance. However, these two parameters are not fixed and change along with the temperature and current of the diode. The curves at all of the possible temperatures are not provided by the manufacturers. In most cases, only curves at 25°C and 150°C are found in the data sheet.
- b. The $R_{DS,ON}$ of the MOSFET varies along with its junction temperature and current. However, the PCB parasitic resistance cannot be ignored when using an extremely low $R_{DS,ON}$ device (such as 10 mΩ), which makes it difficult to estimate the power dissipation on active-bridge line rectification.

 


Figure 15 The equivalent circuit and the conduction loss from $R_{DS,ON}$ of the power MOSFET

2.1.2 PFC efficiency estimation with active bridge

Figure 16 and Figure 17 present the efficiency simulated curves as a function of the output load for a standard PFC with active-line rectification at high- and low-line respectively. Moreover, an efficiency comparison is done between the PFC solution without and with active bridge using different $R_{DS,ON}$, i.e. 22 mΩ, 40 mΩ and 65 mΩ. Estimation of bridge losses is done using the formula described in previous subsection. Simulation results can then be compared to experimental measurements of the next section in order to understand the limits of the model.

PFC efficiency increase with active bridge

 


Figure 16 Simulation results with (22 mΩ, 40 mΩ, 65 mΩ) and without active-bridge line rectification at high-line

 


Figure 17 Simulation results with (22 mΩ, 40 mΩ, 65 mΩ) and without active-bridge line rectification at low-line

PFC efficiency increase with active bridge

2.2 PFC efficiency measurements with active bridge

The efficiency measurements are performed on the **EVAL_2K4W_ACT_BRD_S7** using active-bridge daughter cards with different $R_{DS,ON}$, i.e. 22 mΩ, 40 mΩ and 65 mΩ, and without any heatsink attached to the bridge (even in the case that the active bridge is not plugged in). Load is changed through a DC electronic load and the output voltage is kept constant by the PFC at around 390 V_{DC}. The fan is supplied internally by the board. As a result its consumption is included in the efficiency measurements.

Results at nominal high-line voltage (230 V_{AC}) are shown in Figure 18. A peak efficiency of 98.6 percent is reached with 22 mΩ active bridge at around half load. From Figure 18 it is also evident that the PFC efficiency with the 22 mΩ active bridge is above 98 percent in almost all the load conditions, keeping a constant delta compared to the diode solution in the range of 0.4 to 0.5 percent. The 40 mΩ active bridge keeps a constant delta compared to the diode solution in the range of 0.4 percent up to half of the maximum load. The 65 mΩ active bridge is close to the one reached with the diode bridge only when the output power is around 2400 W. This means that the major benefit of this kit is given below: 50 percent of the output power.

Measurements at nominal low-line voltage (115 V_{AC}) are reported in Figure 19. A peak efficiency of 97.6 percent is reached with 22 mΩ active bridge at around half load. Similar behavior is experienced compared to high line.

Finally, Figure 20 presents the efficiency gain using the active bridges a) at high-line and b) at low-line.

A peak efficiency improvement of 1.3 percent is reached at low-line with an active-bridge line rectification of 22 mΩ MOSFET. At high-line the delta efficiency peak is around 0.7 percent.

 


Figure 18 Efficiency test result of EVAL_2K4W_ACT_BRD_S7 with 22 mΩ (green line), 40 mΩ (light blue), 65 mΩ (red) active-bridge line rectification and with only the diode bridge (black) at 230 V_{AC}

PFC efficiency increase with active bridge

 


Figure 19 Efficiency test result of EVAL_2K4W_ACT_BRD_S7 with 22 mΩ, 40 mΩ, 65 mΩ full-wave active-bridge line rectification and without active bridge (passive) at 115 V_{AC}

 


Figure 20 Delta efficiency test result of EVAL_2K4W_ACT_BRD_S7: comparison between passive and active bridge at different R_{DS,ON}

PFC efficiency increase with active bridge

2.3 Relay MOSFET impact on PFC efficiency

 


Figure 21 Delta efficiency test result of EVAL_2K4W_ACT_BRD_S7: comparison of relay MOSFETs with different $R_{DS,ON}$

Figure 21 shows the impact of the different solid-state relay MOSFETs on the overall PFC efficiency. Three different $R_{DS,ON}$ 600 V CoolMOS™ S7s are compared in terms of delta efficiency (taking as reference the 65 mΩ results). The experiment in Figure 21 demonstrates that, at high-line, there is a gain of around 0.08 percent of efficiency at full load by using a 22 mΩ device. The gain decreases to 0.04 percent when the device instead has 40 mΩ. At low-line, the advantage of using a lower $R_{DS,ON}$ becomes more evident: 0.25 percent increase with 22 mΩ and 0.08 percent with 40 mΩ.

Furthermore, the benefit of lower-ohmic devices is not limited to efficiency gain, but is also related to a higher current capability during transients and surges with a clear advantage for system reliability.

2.4 Temperature measurements

A long-run test has been performed with thermocouples attached to the main devices of the EVAL_2K4W_ACT_BRD_S7 board. The test has been run for nominal input voltage (230 V_{rms}) as well as the minimum input voltage (90 V_{rms}), which is the worst case for PFC operation. The tested unit was enclosed and the fan was controlled by the bias Flyback supplied from the output voltage of the PFC. Therefore, the results presented in this section provide the thermal performance of the 2400 W active-bridge PFC with S7 MOSFETs introduced in this document at room temperature.

The monitored parts in the thermal test are:

- Ambient temperature
- Diode bridge
- Active bridge
- Heatsink: where both PFC MOSFET and diode are thermally connected to
- PFC choke
- Solid-state relay MOSFET

PFC efficiency increase with active bridge

 


Figure 22 Bridge temperature measurements of EVAL_2K4W_ACT_BRD_S7 at nominal high-line

Figure 22 shows the temperature evolution of the bridge (passive or active) from 10 percent to 100 percent of the output power at high-line (230 Vrms). With a 22 mΩ 600 V CoolMOS™ S7, the active-bridge temperature reaches a maximum of 43°C at full power (2400 W) and room temperature. In the same conditions, 40 and 65 mΩ devices reach 54°C and 63°C respectively. These results justify the removal of the heatsink for the bridge cooling and eventually the employment of a less powerful fan. Moreover, there is enough margin in case the ambient temperature increases.

Figure 23 presents the temperature results at low-line (120 Vrms). With a 22 mΩ 600 V CoolMOS™ S7, the active-bridge temperature reaches a maximum of 55°C at 1200 W. In the same conditions, 40 and 65 mΩ devices reach 63°C and 64°C respectively. When the active bridge is removed, the temperature of the diode bridge is around 73°C.

For completeness, Figure 24 and Figure 25 report the temperature measured on the other main PFC components both at high- and low-line.

Finally, Figure 26 **Error! Reference source not found.** shows an acquisition with the thermocamera at 2400 W.

PFC efficiency increase with active bridge

 


Figure 23 Bridge temperature measurements of EVAL_2K4W_ACT_BRD_S7 at minimum low-line

 


Figure 24 Other PFC devices temperature measurements of EVAL_2K4W_ACT_BRD_S7 at nominal high-line

PFC efficiency increase with active bridge

 


Figure 25 Other PFC devices temperature measurements of EVAL_2K4W_ACT_BRD_S7 at minimum low-line

3 DC-link pre-charge and PFC start-up

3.1 Relay replacement introduction

 


Figure 26 Inrush current device from AC-side to DC-link side

One of the major trends in the power supplies market is increasing power density. One way of achieving higher density is by removing the EM relay and replacing it with a MOSFET.

It is more convenient to move the pre-charge circuit, switching device plus PTC/NTC/power resistor, from the AC-side to the DC-link side (in series with the bulk capacitor), as shown in Figure 26. In this way, not only is the RMS current flowing through the switching device lower, but also the driving circuit can be implemented much more simply, without the need for an isolated driver or bootstrap circuitry.

Moreover, MOSFETs have less volume and weight impact compared to relays. Figure 27a presents a size comparison between a typical EM relay used for PFC applications and a CoolMOS™-based solution in a TOLL package. By using MOSFETs, the volume reduction is around 91 percent. In addition, relays are much heavier: a PCB relay is in the range of 10 g, while a smart switch is in the range of 1 g or even below for small packages [5]. In terms of efficiency (Figure 27b), the advantage of using MOSFETs is more evident at light load (+0.12 percent at 10 percent load), when the coil losses of the relay become significantly dominant compared to the driving losses of the MOSFET. At heavy loads the MOSFET still slightly outperforms the relay if the right $R_{DS,ON}$ is chosen.

 


Figure 27 Size (a) and efficiency (b) comparison between standard mechanical relay at AC-side and CoolMOS™-based solution at DC-side

DC-link pre-charge and PFC start-up

In summary, the major benefits of using MOSFETs in place of relays are:

- Increased power density
- Improved system reliability and robustness
- Improved power dissipation (especially in terms of control losses [5])
- Better EMI behavior during switch-on/off
- Removal of the relay acoustic noise (attractive for TV applications)
- Easier implementation of the diagnosis (relevant for automotive and high-safety applications)

Nevertheless, there are still same challenges to be addressed and solved in the case of employing a pre-charge MOSFET: i.e. device protection in the event of high voltage surge pulse and cost optimization of the solution at overall application level.

3.2 Pre-charge control strategy

The active-bridge CCM PFC demo board implements the inrush current limitation circuit at the DC-link side, for reasons discussed previously. The circuit is composed of a 22mΩ 600 V CoolMOS™ S7 in parallel with a 30 Ω NTC resistor and limits the turn-on inrush current.

When the AC-line is connected to the PFC, the DC-link capacitor starts to be charged with a maximum current limited by the NTC resistance value and after a few hundreds of ms reaches a DC voltage slightly below the peak of the AC voltage. In the meantime the bulk voltage rises, and the bias power supply starts up and provides the 12 V supply to the PFC controller, turning it on.

The control signal for activating the pre-charge MOSFET is realized by an “OR” between two analog signals coming from the Infineon PFC controller ICE3PCS01G: the VB_OK and the PWM signals as shown in Figure 28. VB_OK becomes high once the bulk voltage reaches 95 percent of the rated PFC output voltage while the PWM is the control signal of the main PFC MOSFET. The pre-charge MOSFET is kept high as long as the bulk capacitor is charged at a proper voltage level or the PWM signal is commutating, thus meaning that the PFC is active and boosting the voltage to the target value.

The only VB_OK signal is not enough since it becomes high too late during start-up, leading to additional stress on the pre-charge MOSFET during the start-up phase.

 


Figure 28 Control network of the pre-charge MOSFET

DC-link pre-charge and PFC start-up

3.3 Pre-charge and start-up experimental results

Figure 29 and Figure 30 present the PFC pre-charge and start-up sequence for both high- and low-line respectively. One can see that the inrush CoolMOS™, used in place of the relay, is switched on when the PFC is starting to modulate the PWM signal. During start-up, as long as the bulk voltage is less than 95 percent of the rated one, the internal voltage loop output (current reference) increases from an initial value under soft-start control. This results in a controlled linear increase of the output from 0 A, thus reducing the stress on the external components. Once 95 percent is reached, the soft-start control is released to achieve good regulation and dynamic response.

 


Figure 29 Pre-charge and PFC start-up at 250 V_{AC}

 


Figure 30 Pre-charge and PFC start-up at 120 V_{AC}

AC-Line Drop-Out (ACLDO)

4 AC-Line Drop-Out (ACLDO)

4.1 Test-bench

 


Figure 31 Test-bench for voltage drop-out emulation

The robustness of the active-bridge PFC against AC-Line Drop-Out (ACLDO) events is tested in the worst operating conditions, i.e. AC voltage from 265 V to 0 V during 10/20 ms happening at 90 degrees or 270 degrees, and using a DC electronic load demanding partial or full load at constant power. Test bench is shown in Figure 31.

4.2 Experimental results

Figure 32 shows the results of a 20 ms ACLDO at 75 percent of the load power, where a minimum bulk voltage of 272 V is reached.

 


Figure 32 Voltage drop of 20 ms at 1800 W

AC-Line Drop-Out (ACLDO)

The detail of Figure 33 shows that at the time the AC-line comes back the pre-charge MOSFET is still driven high and it experiences a current peak around 110 A with a pulse duration around 2 μ s.

Figure 34 shows the results of a 10 ms ACLDO at full-load power, where a minimum bulk voltage of 311 V is reached.

 


Figure 33 Zoom: voltage drop of 20 ms at 1800 W

 


Figure 34 Voltage drop of 10 ms at 2400 W

AC-Line Drop-Out (ACLDO)

4.3 Simulation of body diode conduction during ACLDO

Test results in the previous section clearly show that during ACLDO pre-charge MOSFET is kept high by the controller and thus is still conducting during the return of the AC voltage. In case the MOSFET is switched off, the CoolMOS™ body diode will conduct during the hold-up time, while the bulk capacitor is fully supplying the load.

In the simulation test of Figure 35, the body diode of the pre-charge MOSFET is conducting during the 20 ms hold-up time with an output constant current of 8 A. In the worst case of case temperature of 140°C the delta temperature between case and junction is below 2°C, confirming low thermal stress for the device. As long as the AC voltage is back, the load current will be supplied by the PFC and only the bulk capacitor ripple current will flow through the pre-charge MOSFET.

 


Figure 35 Simulation in case of relay CoolMOS™ body diode conducting during voltage drop-out

Surge immunity test

5 Surge immunity test

5.1 Surge specification from the standards

 


Figure 36 Surge voltage waveform according to IEC 61000-4-5

Power-line surges are caused by lightning strikes, load switching, capacitor bank switching, equipment faults, etc.

The methodology for surge testing is well developed and is described by the IEC 61000-4-5 standard [4], which specifies the surge generator output into both open- and short-circuits.

The open-circuit voltage-surge waveform shown in Figure 36 is called the Combination Wave Generator (CWG) 1.2/50 μ s waveform. Another aspect is the number of surge strikes needed for the test. The VDE 0884-11 standard specifies the application of 50 surge strikes, of which 25 are of polarity one, followed by 25 of polarity two.

The ability of devices to withstand such surges is important, because it has a significant impact on field-reliability. In PFC circuits, much of the line surge is attenuated by other components, like spark gaps, MOVs, EMI filters and bus capacitances. The residual surge energy reaching the power MOSFET is dissipated by means of avalanche, making the avalanche rating of the device important, or it can be dissipated by means of current, making the maximum pulse current rating of the device fundamental.

Traditional surge testing for silicon-based power supply applications involves firing surge strikes at specified voltages from 0.5 kV up to 4 kV, depending on the desired rating level. The power supply is typically designed with surge protection components like spark gaps and MOVs that attenuate and dissipate the surge strike. In addition, other components like EMI filters and power-supply capacitances further attenuate the surge voltage. The residual surge waveform reaching the FET is thereby power supply design dependent. In addition, the surge strike can cause system-level failures by stressing other components such as bypass diodes and capacitors.

Surge immunity test

5.2 Surge pulse test bench

 


Figure 37 Surge pulse test bench

The test bench for surge pulse testing is the one presented in Figure 37. The surge generator NSG 3040 is coupled with a standard AC source. CWG of 1.2/50 μ s with a series resistor of 2 Ω is applied by the surge generator to the Line and Neutrals conductors. Only differential mode surge is considered in this application note. The load is a fixed resistor of 120 Ω . Rogowski Coils are used for current measurements.

Surge immunity test

5.3 Surge pulse with AC-line

 


Figure 38 PFC running during surge event

The surge pulse is applied during the positive peak of the AC voltage (at 90° of the sinusoid), as shown by Figure 38, with a pulse amplitude from a minimum of 200 V to a maximum of 4 kV. The Vds (green line) and Vgs (blue) of Figure 38 are related to the pre-charge MOSFET. Input voltage (light blue) and input current (magenta) are captured before the EMI filter.

5.3.1 Without active bridge

Figure 39 and Figure 40 show the results with surge pulse voltage at 1 kV and 2 kV respectively. The active bridge was removed from the **EVAL_2K4W_ACT_BRD_S7** and the only diode bridge was present. No failure has been reported on the board. During the surge pulse the pre-charge MOSFET is always kept on, otherwise all the current would flow through the NTC resistor with the consequence of rising the bulk voltage.

In Figure 39 and Figure 40, the Vds (green line) and Vgs (blue) are related to the pre-charge MOSFET, input voltage (light blue) and input current (magenta) are captured before the EMI filter.

Surge current is completely flowing through the diode rectifier since the active bridge is not present. At 1 kV surge the input current peak is around 300 A. At 2 kV surge the input current peak is around 700 A. Similarly, it happens for the pre-charge MOSFET. At 2 kV surge, the current exceeds the maximum pulse current written in the datasheet of the components. In this case, paralleling of 2 devices could be an option, unless the PFC manufacturer takes the risk of operating the device above the datasheet limits.

Surge immunity test

 


Figure 39 Experimental results of 1 kV surge without active bridge

 


Figure 40 Experimental results of 2 kV surge without active bridge

Surge immunity test

5.3.2 With active bridge

Figure 41 and Figure 42 show the results with surge pulse voltage at 1 kV and 2 kV respectively. The active bridge is plugged in the **EVAL_2K4W_ACT_BRD_S7** and it is parallel with the diode bridge rectifier. No failure has been reported on the board. During the surge pulse the pre-charge MOSFET is always kept on, otherwise all the current would flow through the NTC resistor with the consequence of rising the bulk voltage.

In Figure 41 and Figure 42, the V_{ds} (green line) and I_{ds} (blue) are related to the low-side active bridge MOSFET, input voltage (light blue) and diode bridge current (magenta) are also captured.

Surge current is distributed between active and diode bridge. The active bridge experiences more current than the diode bridge, around 60 percent of the total current. At 1 kV surge the active bridge current peak is around 250 A and the diode bridge one is around 200 A. At 2 kV surge the active bridge current peak is around 350 A and the diode bridge one is around 270 A. As a result, the current doesn't exceed the maximum pulse current of the active bridge MOSFET even at 2 kV.

 


Figure 41 Experimental results of 1 kV surge with active bridge

Surge immunity test

 


Figure 42 Experimental results of 2 kV surge with active bridge

5.4 Influence of EMI filter on surge behavior

EMI filter values influence surge pulse response of the PFC converter. In particular, resonance between differential inductance of the common mode choke and X capacitor might affect the surge current peak.

Figure 43 shows the 2 kV surge pulse response with and without X capacitor C4 (the one between the two common mode chokes). The Vds (green line) of the and Vgs (blue) are related to, input voltage (light blue) and bulk capacitor current (magenta) are reported. With the removal of C4 there is a 200 A decrease in the current.

 


Figure 43 2 kV surge pulse BULK current

Summary

6 Summary

Active-bridge line rectification is a circuit that can improve the efficiency within entire power ranges for high efficiency and high power density in SMPS. It demonstrates a flexible design with different daughter board MOSFET $R_{DS,ON}$ for various efficiency requirements of different applications without any other circuit modification. For high power density adapters with burst mode control and convection cooling, but without internal auxiliary power, active-bridge line rectification does reduce the power loss and temperature of power devices. For server power supplies, active-bridge line rectification helps improve the efficiency and extend the power range with at least 94 percent efficiency. The total power loss reduction and efficiency improvement can be estimated by the simple formulas provided in this application note.

For best performance, the MOSFET $R_{DS,ON}$ plays an important role in this application. Considering the mechanical outline, space and thermal conduction inside power supplies, various MOSFET packages are the key to achieving flexibility for such applications. Infineon provides the lowest MOSFET $R_{DS,ON}$ within the same package and MOSFETs with new top-side cooling SMD packages.


Taking into consideration abnormal conditions and EMC tests, solutions for surge voltage and surge current are necessary for MOSFETs. These are also discussed in this application note. Even when active-bridge line rectification acts as a bridge rectifier, a bridge rectifier is still needed, as when they are used in parallel, higher surge current capabilities are possible for abnormal conditions.

Efficiency improvement results with active-bridge line rectification are demonstrated in a 2400 W PFC.

A schematic of a reference circuit is provided in this application note, so that readers can design and manufacture an active-bridge line rectification board following the concept.

Schematics

7 Schematics

 

Active-bridge CCM PFC demo board based on 600 V CoolMOS™ S7

2400 W 65 kHz high-efficiency and high power density design



Schematics

Figure 44 2400 W CCM PFC main board schematic

 


Figure 45 Active-bridge daughter card schematic

Schematics

 


Figure 46 Bias power supply daughter card schematic

Bill of Materials (BOM)

8 Bill of Materials (BOM)

Table 3 Main board components

| Designator | Comment | Value | Tolerance | Voltage | Description |
|---|---------|------------------------|-------------|---------|-------------------|
| X1 | THT | MKDS 5/3-6, 35-1714955 | | | Connector |
| T4 | SMD | BC817-40 | | 45 V | NPN-transistor |
| T3 | SMD | IPT60R022S7 | | 600 V | N-channel MOSFET |
| T2 | THT | IPZ60R040C7 | | 600 V | N-channel MOSFET |
| T1 | SMD | BC807-40 | | 45 V | PNP-transistor |
| R36, R41 | SMD | 25k5 | 1 percent | | Resistor |
| R35, R46 | SMD | 470 k | 1 percent | | Resistor |
| R31, R34 | SMD | 200 k | 1 percent | | Resistor |
| R30 | SMD | 30k2 | 1 percent | | Resistor |
| R28 | SMD | 330 k | 1 percent | | Resistor |
| R27, R33 | SMD | 68 k | 1 percent | | Resistor |
| R18, R25 | SMD | 510 R | 1 percent | | Resistor |
| R17, R24 | SMD | 15 R | 1 percent | | Resistor |
| R13, R14, R32 | SMD | 3k3 | 1 percent | | Resistor |
| R12, R15, R20, R29 | SMD | 100 k | 1 percent | | Resistor |
| R10, R11 | SMD | 270 R | 1 percent | | Resistor |
| R9, R22, R23, R26, R37, R38, R39, R40, R42, R43, R44, R45 | SMD | 1 Meg | 1 percent | | Resistor |
| R7, R8, R16, R19, R21 | SMD | 4R7 | 1 percent | | Resistor |
| R6 | SMD | R005 | 1 percent | | Shunt resistor |
| R1, R2, R3, R4, R5 | SMD | 150 k | 1 percent | | Resistor |
| NTC1 | THT | 30 R | ±20 percent | | NTC resistor |
| MOV1 | THT | V320LA20AP | | | Varistor |
| L4 | THT | MG10000850 | | | Inductor |
| L3 | THT | 5 mH | | | Common-mode choke |
| L1, L2 | THT | 2.5 mH | | | Common-mode choke |
| IC3 | SMD | LT1013DDG4 | | | Dual-precision |

Active-bridge CCM PFC demo board based on 600 V CoolMOS™ S7

2400 W 65 kHz high-efficiency and high power density design



Bill of Materials (BOM)

| Designator | Comment | Value | Tolerance | Voltage | Description |
|--------------------|---------|------------------|------------|---------------------|-------------------------------|
| | | | | | operational amplifier |
| IC2 | SMD | ICE3PCS01G | | | Standalone CCM PFC controller |
| IC1 | SMD | 1EDN8550B | | | Gate-driver IC |
| H2 | THT | HT100002000 | | | Heatsink |
| H1 | THT | HT200002000 | | | Heatsink |
| F1 | THT | 15 A | | | Fuse |
| D6 | SMD | 18 V | | 18 V | Zener diode |
| D5 | SMD | BAT165 | | 40 V | Schottky diode |
| D3, D4, D7 | SMD | MURS360BT3G | | 600 V | Standard diode |
| D2 | THT | IDH12G65C6 | | 650 V | SiC diode |
| D1 | SMD | S8KCDICT | | 800 V | Standard diode |
| C18 | SMD | 470 nF | X7R | 25 V | Ceramic capacitor |
| C17, C20, C22, C23 | SMD | 1 nF | X7R | 50 V | Ceramic capacitor |
| C15 | THT | 820 μ F | 20 percent | 450 V | Polarized capacitor |
| C14, C21 | SMD | 100 nF | X7R | 25 V | Ceramic capacitor |
| C12 | SMD | 4n7 | X7R | 50 V | Ceramic capacitor |
| C11 | SMD | 470 pF | X7R | 50 V | Ceramic capacitor |
| C10, C13, C19 | SMD | 1 μ F | X7R | 25 V | Ceramic capacitor |
| C6, C7 | THT | 2.2 μ F | 5 percent | 450 V _{DC} | Foil capacitor |
| C4 | THT | 3.3 μ F x2 | 10 percent | 305 V _{AC} | Foil capacitor |
| C16 | THT | 0.33 μ F x2* | 20 percent | 275 V _{AC} | Foil capacitor |
| C3, C5 | THT | 0.68 μ F x2 | 20 percent | 275 V _{AC} | Foil capacitor |
| C1, C2, C8, C9 | THT | 4.7 nF | Y2 | 300 V | Ceramic capacitor |
| BR1 | THT | LVB2560 | | 600 V | |

*Capacitance value of C16 has been decreased due to mechanical constraints. In order to have better EMI performance, consider increasing this value.

Bill of Materials (BOM)

Table 4 Active-bridge daughter card components

| Designator | Comment | Value | Tolerance | Voltage | Description |
|---|---------|------------------|-----------|---------|--------------------|
| C1, C3 | SMD | 4.7 μ F | X7R | 25 V | Ceramic capacitor |
| C2 | SMD | 22 nF | X7R | 50 V | Ceramic capacitor |
| C4, C5, C6 | SMD | 1 μ F | X7R | 25 V | Ceramic capacitor |
| D1, D2 | SMD | MURS360BT3G | | 600 V | Standard diode |
| IC1 | SMD | 2EDF7275F | | | Integrated circuit |
| IC2 | SMD | IR11688S | | | Integrated circuit |
| Q1, Q2, Q3, Q4 | SMD | IPT60R040S7 | | 600 V | N-channel MOSFET |
| R1, R2, R5, R6, | SMD | 560 R | 1 percent | | Resistor |
| R12, R13 | SMD | 10 k | 1 percent | | Resistor |
| R3, R4, R7, R8, R14 | SMD | 47 k | 1 percent | | Resistor |
| R9, R10 | SMD | 47 R | 1 percent | | Resistor |
| R11 | SMD | 3 k | 1 percent | | Resistor |
| R15 | SMD | 100 k | 1 percent | | Resistor |
| R16 | SMD | 150 R | 1 percent | | Resistor |
| R17, R18 | SMD | 100 R | 1 percent | | Resistor |
| T1, T2 | SMD | BSP300H6327XUSA1 | | 800 V | N-channel MOSFET |
| R9, R22, R23, R26, R37, R38, R39, R40, R42, R43, R44, R45 | SMD | 1 Meg | 1 percent | | Resistor |

Table 5 Bias power supply daughter card components

| Designator | Qty | Description | Manufacturer | Part number |
|------------|-----|--|--------------|-------------|
| C1 | 1 | Ceramic capacitor, 10 pF, 1 kV, NP0, CAP1206 | Kemet | 1702125 |
| C5 | 1 | Ceramic capacitor, 22 nF, 1 kV, CAP1210 | Murata | 2456116 |
| C6, C9 | 2 | Ceramic capacitor, 1 μ F, 25 V, X7R, CAP1206 | | |

Active-bridge CCM PFC demo board based on 600 V CoolMOS™ S7

2400 W 65 kHz high-efficiency and high power density design



Bill of Materials (BOM)

| Designator | Qty | Description | Manufacturer | Part number |
|---------------|-----|---|--------------|----------------|
| C7 | 1 | Electrolytic capacitor, 150 µF, 20 V | Kemet | |
| C8 | 1 | Electrolytic capacitor, 220 µF, 16 V | Kemet | 1793863 |
| C11 | 1 | Ceramic capacitor, 22 µF, 25 V, X7R, CAP1210 | | |
| C12 | 1 | Ceramic capacitor, 0.1 µF, 25 V, X7R, CAP0805 | | |
| C13 | 1 | Ceramic capacitor, 1 nF, 25 V, NP0, CAP0805 | | |
| C14 | 1 | Ceramic capacitor, 470 pF, 25 V, NP0, CAP0805 | | |
| C15 | 1 | Ceramic capacitor, 1.5 nF, 25 V, X7R, CAP0805 | | |
| D1 | 1 | Schottky diode, BZX384-B2V4, SOD323 | Nexperia | 1727-3647-1-ND |
| D2 | 1 | Schottky diode, BZX384-B18, SOD323 | Nexperia | |
| D9, D11 | 2 | Standard diode, MBRS1100T3, SMB/DO-214AA | | 2317670 |
| D12, D14 | 2 | Medium-power AF Schottky diode, BAT165, S0D250X125X110-2N | Infineon | 1056502 |
| D16 | 1 | Schottky diode, BZX384-B12, SOD323 | Nexperia | |
| IC2 | 1 | QR Flyback controller, ICE5QSAG, SOIC8 | Infineon | ICE5QSAG |
| LED1 | 1 | LED, 2.9 V, LED-0603R | Rohm | 2762564 |
| Q2 | 1 | N-channel MOSFET, BSS138N, SOT23R | Infineon | 2432717 |
| R1 | 1 | Resistor, 2 k, RES0805W | Vishay | 1469884 |
| R2 | 1 | Resistor, 33 R, RES0805R | Vishay | 1738939 |
| R18 | 1 | Resistor, 22 k, RES0805W | Vishay | 1469896 |
| R19, R22, R24 | 3 | Resistor, 3.3 M, RES0805W | | |
| R20, R23, R25 | 3 | Resistor, 10 M, RES0805W | | |
| R26 | 1 | Resistor, 22 R, RES0805W | | |
| R27 | 1 | Resistor, 3R3, RES0805W | Vishay | 2413965 |
| R29 | 1 | Resistor, 150 k, RES0805W | | |
| R30 | 1 | Resistor, 47 R, RES0805W | | |
| R31 | 1 | Resistor, 1 k, RES0805W | | |

**Active-bridge CCM PFC demo board based on 600 V CoolMOS™ S7
2400 W 65 kHz high-efficiency and high power density design**



Bill of Materials (BOM)

| Designator | Qty | Description | Manufacturer | Part number |
|-------------------|------------|---------------------------|---------------------|--------------------|
| R32 | 1 | Resistor, 10 k, RES0805W | | |
| T2 | 1 | MOSFET, 950 V CoolMOS™ P7 | Infineon | IPU95R3K7P7 |
| TF2 | 1 | Flyback transformer | | 8066.0103.030 |
| X3 | 1 | Pin header, 5-pin | Samtec | 2041577 |
| X4 | 1 | Pin header, 3-pin | Samtec | 2041576 |

References

9 References

- [1] “PFC demo board based on CoolMOS™ P7 600 V: 800 W 65 kHz platinum server design”, AN_201703_PL52_016.
- [2] “6 W bias supply using the new 950 V CoolMOS™ P7, ICE5QSAG QR Flyback controller, and snubberless Flyback for improved auxiliary power supply efficiency and form-factor”, AN_1801_PL52_1803_160336
- [3] “Data sheet – IR11688S”, from Infineon
- [4] “Design notes control IC SmartRectifier™ IR11688”, application note from Infineon
- [5] “Relay replacement within automotive power distribution. Smart switch versus relay: detailed comparison”, application note Z8F65515545

Revision history

Revision history

| Document version | Date of release | Description of changes |
|-------------------------|------------------------|-------------------------------|
| V 1.0 | 13.09.2019 | First release |
| | | |
| | | |

Trademarks

All referenced product or service names and trademarks are the property of their respective owners.

Edition 2020-02-28

Published by

Infineon Technologies AG

81726 Munich, Germany

© 2020 Infineon Technologies AG.

All Rights Reserved.

Do you have a question about this document?

Email: erratum@infineon.com

Document reference

AN_1905_PL52_1905_101502

IMPORTANT NOTICE

The information contained in this application note is given as a hint for the implementation of the product only and shall in no event be regarded as a description or warranty of a certain functionality, condition or quality of the product. Before implementation of the product, the recipient of this application note must verify any function and other technical information given herein in the real application. Infineon Technologies hereby disclaims any and all warranties and liabilities of any kind (including without limitation warranties of non-infringement of intellectual property rights of any third party) with respect to any and all information given in this application note.

The data contained in this document is exclusively intended for technically trained staff. It is the responsibility of customer's technical departments to evaluate the suitability of the product for the intended application and the completeness of the product information given in this document with respect to such application.

For further information on the product, technology, delivery terms and conditions and prices please contact your nearest Infineon Technologies office (www.infineon.com).

WARNINGS

Due to technical requirements products may contain dangerous substances. For information on the types in question please contact your nearest Infineon Technologies office.

Except as otherwise explicitly approved by Infineon Technologies in a written document signed by authorized representatives of Infineon Technologies, Infineon Technologies' products may not be used in any applications where a failure of the product or any consequences of the use thereof can reasonably be expected to result in personal injury.